

Spartan6 - DSP48A1-Project

Digital Designer: George Safwat Wasfy

Presented for:

Digital Design Using Verilog &FPGA Flow Using VIVADO Diploma

Under supervision of: Eng. Kareem Waseem

 


Table of Contents

1-RTL code	3
First: Instantiation Modules	3
Second: Spartan6 - DSP48A1-Design	4
Inputs, Outputs &Parameters:	4
Instantiations	5
2-Testbench-code	7
3-Do file.	11
4-QuestaSim	12
5-QuestaLint	13
6-Synthesize	14
Elaborated Design:	14
Synthesized design:	14
Report timing summary:	16
Utilization summary:	16
7-Implementation	17
Report timing summary:	18
Utilization summary:	18

1-RTL code

First: Instantiation Modules

```
module Mux_Reg(in,clk,out,rst,CE,sel);
parameter input_size=18,RSTTYPE="SYNC";
input [input_size-1:0]in;
input clk,rst,CE,sel;
output [input_size-1:0] out;
reg [input_size-1:0]regs;

assign out= (sel==1)?  regs:in;

generate
|   if(RSTTYPE=="SYNC")begin
always @(posedge clk) begin
|   |   if(rst)
regs<=0;
else begin
|   |   if(CE)
regs<=in;
end
end
|   end
else begin
if(RSTTYPE=="ASYNC")begin
always @(posedge clk or posedge rst) begin
|   |   if(rst)
regs<=0;
else begin
|   |   if(CE)
regs<=in;
end
|   end
end
endgenerate
endmodule
```

```
module Muxb(in0,in1,b0);
parameter sel="Direct";
input [17:0]in0;
input [17:0]in1;
output [17:0]b0;                                //Input B
assign b0= (sel=="Direct"?  in0:(sel=="CASCADE"?  in1:0;
endmodule
```

```
module mux2(sel,in0,in1,out);
input [17:0] in0,in1; //in0=pre  in1=b0_out
input sel;
output [17:0] out;           //opmode[4]
assign out=(sel==0)? in1:in0;
endmodule
```

```
module mux_cin(in0,in1,out);
parameter sel="OPMODE5";
input in0,in1;
output out;           //opmode[5]
assign out=(sel=="OPMODE5"? in0:in1;
endmodule
```

```
module mux4(in0,in1,in2,in3,out,sel);
input [47:0]in0,in1,in2;
input [1:0]sel;           //for Mux Z
output [47:0]out;
input in3;
assign out=(sel==0)? in3:(sel==1)? in2:(sel==2)? in1:in0;
endmodule
```

```
module mux4_x(in0,in1,in2,in3,out,sel);
input [47:0]in0,in1;
input [35:0]in2;
input [1:0]sel;           //for Mux X
output [47:0]out;
input in3;
assign out=(sel==0)? in3:(sel==1)? in2:(sel==2)? in1:in0;
endmodule
```

Second: Spartan6 - DSP48A1-Design

Inputs, Outputs &Parameters:


```
module DSP(A,B,C,D,CARRYIN,M,P,CARRYOUT,
CARRYOUTF,clk,opmode,cea,ceb,cec,cecarryin,
ced,cem,ceopmode,cep,rsta,rstb,rstc,rstcarryin,
rstd,rstm,rstopmode,rstp,BCOUT,PCIN,PCOUT,BCIN);
parameter A0REG=0,B0REG=0,A1REG=1,B1REG=1,CREG=1, DREG=1, MREG=1,
PREG=1, CARRYINREG=1,CARRYOUTREG=1,OPMODEREG=1,
CARRYINSEL="OPMODE5",B_INPUT="DIRECT",RSTTYPE="SYNC";
```

```
input CARRYIN,clk,cea,ceb,cec,cecarryin,
ced,cem,ceopmode,cep,rsta,rstb,rstc,rstcarryin,
rstd,rstm,rstopmode,rstp;
input [7:0]opmode;
input [17:0]A,B,D,BCIN;
input [47:0]C,PCIN;
output [47:0]P,PCOUT;
output [35:0]M;
output reg CARRYOUT;
output CARRYOUTF;
output [17:0]BCOUT;
```

```
wire [17:0]a,a1_out,d,b0,b0_out,b1,b1_out;
reg [17:0]pre_add_sub;
reg [48:0]post_add_sub;
wire [35:0]M_out;
reg [35:0]M_in;
wire [47:0]c,z,x;
wire [7:0]opmode_out;
wire cyi,cyi_out,cyo_out;
```

Blue signals are Internal Wires.

Red signals are Internal Registers.

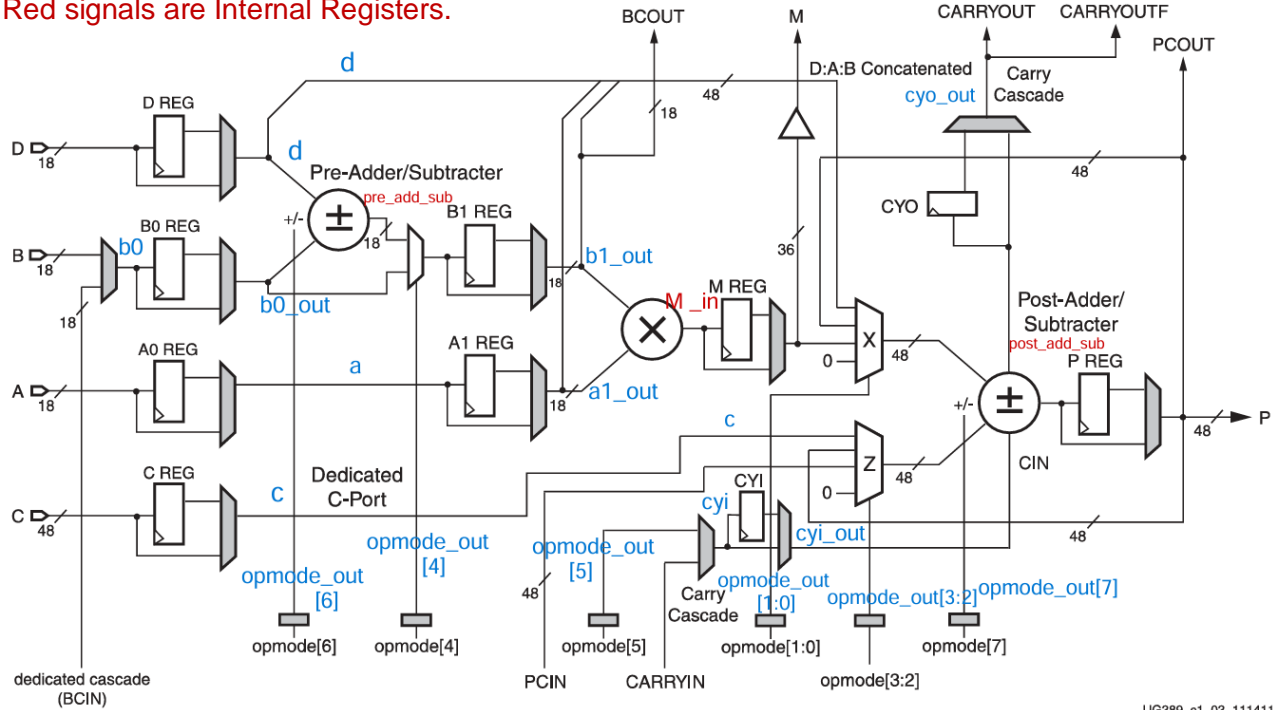

UG389_c1_03_111411

Figure 1-3: DSP48A1 Slice

Instantiations

```
//Input A
Mux_Reg a0(.in(A),.clk(clk),.out(a),.rst(rsta),.CE(cea),.sel(A0REG));
Mux_Reg a1(.in(a),.clk(clk),.out(a1_out),.rst(rsta),.CE(cea),.sel(A1REG));
//Input B
Muxb B_in(.in0(B),.b0(b0),.in1(BCIN));
Mux_Reg B0(.in(b0),.clk(clk),.out(b0_out),.rst(rstb),.CE(ceb),.sel(B0REG));
mux2 b_in(.sel(opmode_out[4]),.in0(pre_add_sub),.in1(b0_out),.out(b1));
Mux_Reg B1(.in(b1),.clk(clk),.out(b1_out),.rst(rstb),.CE(ceb),.sel(B1REG));
//Input C
Mux_Reg c(.input_size(48)c_in(.in(C),.clk(clk),.out(c),.rst(rstc),.CE(cec),.sel(CREG));
//Input D
Mux_Reg d_in(.in(D),.clk(clk),.out(d),.rst(rstd),.CE(ced),.sel(DREG));
//Output P
Mux_Reg p(.input_size(48)p(.in(post_add_sub),.clk(clk),.out(P),.rst(rstp),.CE(cep),.sel(PREG));
//M
Mux_Reg m(.input_size(36)m(.in(M_in),.clk(clk),.out(M_out),.rst(rstm),.CE(cem),.sel(MREG));
//Opmodes
Mux_Reg op1(.in(opmode[1:0]),.clk(clk),.out(opmode_out[1:0]),.rst(rstopmode),.CE(ceopmode),.sel(OPMODEREG));
Mux_Reg op2(.in(opmode[3:2]),.clk(clk),.out(opmode_out[3:2]),.rst(rstopmode),.CE(ceopmode),.sel(OPMODEREG));
Mux_Reg op4(.in(opmode[4]),.clk(clk),.out(opmode_out[4]),.rst(rstopmode),.CE(ceopmode),.sel(OPMODEREG));
Mux_Reg op5(.in(opmode[5]),.clk(clk),.out(opmode_out[5]),.rst(rstopmode),.CE(ceopmode),.sel(OPMODEREG));
Mux_Reg op6(.in(opmode[6]),.clk(clk),.out(opmode_out[6]),.rst(rstopmode),.CE(ceopmode),.sel(OPMODEREG));
Mux_Reg op7(.in(opmode[7]),.clk(clk),.out(opmode_out[7]),.rst(rstopmode),.CE(ceopmode),.sel(OPMODEREG));
//CARRYIN
mux_cin cin(.in0(opmode[5]),.in1(CARRYIN),.out(cyi));
Mux_Reg cyi(.in(cyi),.clk(clk),.out(cyi_out),.rst(rstcarryin),.CE(ceopmode),.sel(CARRYINREG));
//CARRYOUT
Mux_Reg cyo(.in(post_add_sub[48]),.clk(clk),.out(cyo_out),.rst(rstcarryin),.CE(ceopmode),.sel(CARRYOUTREG));
//MUX_z
mux4 MUXz(.in0(c),.in1(PCIN),.in2(P),.in3(0),.out(z),.sel(opmode[3:2]));
//MUX_x
mux4_x MUXx(.in0({d[11:0],a1_out,b1_out}),.in1(P),.in2(M_out),.in3(0),.out(x),.sel(opmode[1:0]));
```

```

always @(posedge clk) begin
case({opmode[7],opmode[6]})
2'b00:begin
pre_add_sub= d + b0_out;
M_in= b1_out*a1_out ;
post_add_sub=x+z;
CARRYOUT=cyo_out;
end

2'b01:begin
pre_add_sub=d-b0_out;
M_in=b1_out*a1_out;
post_add_sub=z+x;
CARRYOUT=cyo_out;
end

2'b10:begin
pre_add_sub=d+b0_out;
M_in=b1_out*a1_out;
post_add_sub=z-(x+cyi_out);
CARRYOUT=cyo_out;
end

2'b11:begin
pre_add_sub=d-b0_out;
M_in=b1_out*a1_out;
post_add_sub=z-(x+cyi_out);
CARRYOUT=cyo_out;
end
endcase

end
assign BCOUT=b1_out;
assign M=~(~M_out);
assign CARRYOUTF=CARRYOUT;
assign PCOUT=P;

endmodule

```

2-Testbench-code

```
module DSP_tb();
parameter A0REG=0,B0REG=0,A1REG=1,B1REG=1,CREG=1, DREG=1, MREG=1,
PREG=1, CARRYINREG=1,CARRYOUTREG=1,OPMODEREG=1,
CARRYINSEL="OPMODE5",B_INPUT="DIRECT",RSTTYPE="SYNC";

reg CARRYIN,clk,cea,ceb,cec,cecarryin,
ced,cem,ceopmode,cep,rsta,rstb,rstc,rstcarryin,
rstd,rstm,rstopmode,rstp;

reg [7:0]opmode;
reg [17:0]A,B,D;
reg [47:0]C,PCIN;
reg [17:0]BCIN;

wire [47:0]P,PCOUT;
wire [35:0]M;
wire CARRYOUT;
wire CARRYOUTF;
wire [17:0]BCOUT;

DSP DSP_test(.A(A),.B(B),.C(C),.D(D),.CARRYIN(CARRYIN),.M(M),.P(P),.CARRYOUT(CARRYOUT),
.CARRYOUTF(CARRYOUTF),.clk(clk),.opmode(opmode),.cea(cea),.ceb(ceb),.cec(cec),.cecarryin(cecarryin),
.ced(ced),.cem(cem),.ceopmode(ceopmode),.cep(cep),.rsta(rsta),.rstb(rstb),.rstc(rstc),.rstcarryin(rstcarryin),
.rstd(rstd),.rstm(rstm),.rstopmode(rstopmode),.rstp(rstp),.BCOUT(BCOUT),.PCIN(PCIN),.PCOUT(PCOUT));

initial begin
clk=1;
forever #1 clk=~clk;
end
```

```

integer i;
initial begin
//Test reset
rsta=1;
rstb=1;
rstc=1;
rstcarryin=1;
rstd=1;
rstm=1;
rstopmode=1;
rstp=1;

cea=0;
ceb=0;
cec=0;
cecarryin=0;
ced=0;
cem=0;
ceopmode=0;
cep=0;

A=$random;
B=$random;
C=$random;
D=$random;
opmode=$random;
CARRYIN=$random;
BCIN=$random;
PCIN=$random;
repeat (7) @(negedge clk);

if(P!=0)begin
$display("Error in Design");
$stop;
end

```



```

rsta=0;
rstb=0;
rstc=0;
rstcarryin=0;
rstd=0;
rstm=0;
rstopmode=0;
rstp=0;

cea=1;
ceb=1;
cec=1;
cecarryin=1;
ced=1;
cem=1;
ceopmode=1;
cep=1;

for(i=0;i<10;i=i+1)begin
//test addition
A=$urandom_range(0,1000);
B=$urandom_range(0,1000);
C=$urandom_range(0,1000);
D=$urandom_range(0,1000);
opmode=8'b00111101;
CARRYIN=$random;
BCIN=$random;
PCIN=$random;
repeat (7) @(negedge clk);

```

```

//test subtraction
A=$urandom_range(0,1000);
B=$urandom_range(0,1000);
C=$urandom_range(0,1000);
D=$urandom_range(0,1000);
opmode=8'b11111101;
CARRYIN=$random;
BCIN=$random;
PCIN=$random;
repeat (7) @(negedge clk);

//test subtraction then addition

A=$urandom_range(0,1000);
B=$urandom_range(0,1000);
C=$urandom_range(0,1000);
D=$urandom_range(0,1000);
opmode=8'b01111101;
CARRYIN=$random;
BCIN=$random;
PCIN=$random;
repeat (7) @(negedge clk);

//test addition then subtraction
A=$urandom_range(0,1000);
B=$urandom_range(0,1000);
C=$urandom_range(0,1000);
D=$urandom_range(0,1000);
opmode=8'b10111101;
CARRYIN=$random;
BCIN=$random;
PCIN=$random;
repeat (7) @(negedge clk);

```

```

//Test all cases
A=$random;
B=$random;
C=$random;
D=$random;
opmode=$random;
CARRYIN=$random;
BCIN=$random;
PCIN=$random;
repeat (7) @(negedge clk);

end
$stop;

end
initial begin
    $monitor("A=%d,B=%d,BCOUT=%d,C=%d,D=%d,opmode=%b,P=%d,PCOUT=%d,CARRYOUT=%d,CARRYOUTF=%d",A,B,C,D,BCOUT,opmode,P,PCOUT,CARRYOUT,CARRYOUTF,);
end
endmodule

```


3-Do file

```

vlib work
vlog DSP.v DSP_tb.v MUX_REG.v
vsim -voptargs=+acc work.DSP_tb
add wave *
run -all

```

4-QuestaSim

 

Transcript

```
# A= 188,B= 844,BCOOUT= 555,C= 48,D= 0,opmode=00111101,P= 0,PCOUT= 0,CARRYOUT=0,CARRYOUTF=0
# A= 188,B= 844,BCOOUT= 555,C= 48,D= 844,opmode=00111101,P= 0,PCOUT= 0,CARRYOUT=0,CARRYOUTF=0
# A= 188,B= 844,BCOOUT= 555,C= 48,D= 892,opmode=00111101,P= 555,PCOUT= 555,CARRYOUT=0,CARRYOUTF=0
# A= 188,B= 844,BCOOUT= 555,C= 48,D= 892,opmode=00111101,P= 159227,PCOUT= 159227,CARRYOUT=0,CARRYOUTF=0
# A= 188,B= 844,BCOOUT= 555,C= 48,D= 892,opmode=00111101,P= 168251,PCOUT= 168251,CARRYOUT=0,CARRYOUTF=0
# A= 296,B= 710,BCOOUT= 539,C= 930,D= 892,opmode=11111101,P= 168251,PCOUT= 168251,CARRYOUT=0,CARRYOUTF=0
# A= 296,B= 710,BCOOUT= 539,C= 930,D= 261482,opmode=11111101,P=281474976543514,PCOUT=281474976543514,CARRYOUT=0,CARRYOUTF=0
# A= 296,B= 710,BCOOUT= 539,C= 930,D= 220,opmode=11111101,P=281474976543498,PCOUT=281474976543498,CARRYOUT=1,CARRYOUTF=1
# A= 296,B= 710,BCOOUT= 539,C= 930,D= 220,opmode=11111101,P=281474976447162,PCOUT=281474976447162,CARRYOUT=1,CARRYOUTF=1
# A= 296,B= 710,BCOOUT= 539,C= 930,D= 220,opmode=11111101,P=281474899312522,PCOUT=281474899312522,CARRYOUT=1,CARRYOUTF=1
# A= 296,B= 710,BCOOUT= 539,C= 930,D= 220,opmode=11111101,P=281474976646074,PCOUT=281474976646074,CARRYOUT=1,CARRYOUTF=1
# A= 880,B= 868,BCOOUT= 665,C= 929,D= 220,opmode=01111101,P=281474976646074,PCOUT=281474976646074,CARRYOUT=1,CARRYOUTF=1
# A= 880,B= 868,BCOOUT= 665,C= 929,D= 62,opmode=01111101,P= 65659,PCOUT= 65659,CARRYOUT=1,CARRYOUTF=1
# A= 880,B= 868,BCOOUT= 665,C= 929,D= 61,opmode=01111101,P= 65785,PCOUT= 65785,CARRYOUT=0,CARRYOUTF=0
# A= 880,B= 868,BCOOUT= 665,C= 929,D= 61,opmode=01111101,P= 194265,PCOUT= 194265,CARRYOUT=0,CARRYOUTF=0
# A= 880,B= 868,BCOOUT= 665,C= 929,D= 61,opmode=01111101,P= 55225,PCOUT= 55225,CARRYOUT=0,CARRYOUTF=0
# A= 880,B= 868,BCOOUT= 665,C= 929,D= 61,opmode=01111101,P= 54345,PCOUT= 54345,CARRYOUT=0,CARRYOUTF=0
# A= 82,B= 189,BCOOUT= 619,C= 409,D= 61,opmode=10111101,P= 54345,PCOUT= 54345,CARRYOUT=0,CARRYOUTF=0
# A= 82,B= 189,BCOOUT= 619,C= 409,D= 1118,opmode=10111101,P=281474976657640,PCOUT=281474976657640,CARRYOUT=0,CARRYOUTF=0
# A= 82,B= 189,BCOOUT= 619,C= 409,D= 598,opmode=10111101,P=281474976657594,PCOUT=281474976657594,CARRYOUT=1,CARRYOUTF=1
# A= 82,B= 189,BCOOUT= 619,C= 409,D= 598,opmode=10111101,P=281474976706272,PCOUT=281474976706272,CARRYOUT=1,CARRYOUTF=1
# A= 82,B= 189,BCOOUT= 619,C= 409,D= 598,opmode=10111101,P=281474976619598,PCOUT=281474976619598,CARRYOUT=1,CARRYOUTF=1
# A= 82,B= 189,BCOOUT= 619,C= 409,D= 598,opmode=10111101,P=281474976662238,PCOUT=281474976662238,CARRYOUT=1,CARRYOUTF=1
# A=185874,B= 56207,BCOOUT= 2033215986,C=169678,D= 598,opmode=11101000,P=281474976662238,PCOUT=281474976662238,CARRYOUT=1,CARRYOUTF=1
# A=185874,B= 56207,BCOOUT= 2033215986,C=169678,D= 56207,opmode=11101000,P=281474415601852,PCOUT=281474415601852,CARRYOUT=1,CARRYOUTF=1
# A=185874,B= 56207,BCOOUT= 2033215986,C=169678,D= 56207,opmode=11101000,P=281474415601852,PCOUT=281474415601852,CARRYOUT=0,CARRYOUTF=0
# A= 841,B= 747,BCOOUT= 664,C= 846,D= 56207,opmode=00111101,P=281474415601852,PCOUT=281474415601852,CARRYOUT=0,CARRYOUTF=0
# A= 841,B= 747,BCOOUT= 664,C= 846,D= 170425,opmode=00111101,P= 12480635904,PCOUT= 12480635904,CARRYOUT=0,CARRYOUTF=0
# A= 841,B= 747,BCOOUT= 664,C= 846,D= 1593,opmode=00111101,P= 10447420582,PCOUT= 10447420582,CARRYOUT=0,CARRYOUTF=0
# A= 841,B= 747,BCOOUT= 664,C= 846,D= 1593,opmode=00111101,P= 628891,PCOUT= 628891,CARRYOUT=0,CARRYOUTF=0
# A= 841,B= 747,BCOOUT= 664,C= 846,D= 1593,opmode=00111101,P= 143328089,PCOUT= 143328089,CARRYOUT=0,CARRYOUTF=0
# A= 841,B= 747,BCOOUT= 664,C= 846,D= 1593,opmode=00111101,P= 1340377,PCOUT= 1340377,CARRYOUT=0,CARRYOUTF=0
# A= 502,B= 288,BCOOUT= 304,C= 446,D= 1593,opmode=11111101,P= 1340377,PCOUT= 1340377,CARRYOUT=0,CARRYOUTF=0
run
# A= 502,B= 288,BCOOUT= 304,C= 446,D= 558,opmode=11111101,P=281474975371606,PCOUT=281474975371606,CARRYOUT=0,CARRYOUTF=0
# A= 502,B= 288,BCOOUT= 304,C= 446,D= 158,opmode=11111101,P=281474975371246,PCOUT=281474975371246,CARRYOUT=1,CARRYOUTF=1
# A= 502,B= 288,BCOOUT= 304,C= 446,D= 158,opmode=11111101,P=281474975911273,PCOUT=281474975911273,CARRYOUT=1,CARRYOUTF=1
# A= 502,B= 288,BCOOUT= 304,C= 446,D= 158,opmode=11111101,P=281474976430843,PCOUT=281474976430843,CARRYOUT=1,CARRYOUTF=1
# A= 502,B= 288,BCOOUT= 304,C= 446,D= 158,opmode=11111101,P=281474976631643,PCOUT=281474976631643,CARRYOUT=1,CARRYOUTF=1
```

5-QuestaLint

Questa Lint 2021.1 (...Users/Legion/Desktop/Project_DSP/lint.db)

File Edit View Schematic Window Help

Design C:\Users\Legion\Desktop\Project_DSP\DSP.v [DSP]

Search: Type Search...

Instance DSP (21) DSP

```

1 module DSP(A,B,C,D,CARRYIN,M,P,CARRYOUT,
2 CARRYOUTF,clk,opmode,cea,ceb,cec,cecarryin,
3 ced,cem,ceopmode,cep,rsta,rstb,rstc,rstcarryin,
4 rstd,rstm,rstopmode,rstp,BCOUT,PCIN,PCOUT,BCIN);
5 parameter A0REG=0,B0REG=0,A1REG=1,B1REG=1,CREG=1, DREG=1, MREG=1,
6 PREG=1, CARRYINREG=1,CARRYOUTREG=1,OPMODERE=1,
7 CARRYINSEL="OPMODE5",B_INPUT="DIRECT",RSTTYPE="SYNC";
8
9
10 input CARRYIN,clk,cea,ceb,cec,cecarryin,
11 ced,cem,ceopmode,cep,rsta,rstb,rstc,rstcarryin,
12 rstd,rstm,rstopmode,rstp;
13 input [7:0]opmode;
14 input [17:0]A,B,D,BCIN;
15 input [47:0]C,PCIN;
16 output [47:0]P,PCOUT;
17 output [35:0]M;
18 output reg CARRYOUT;
19 output CARRYOUTF;
20 output [17:0]BCOUT;
21
22 wire [17:0]a,a1_out,d,b0,b0_out,b1,b1_out;
23 reg [17:0]pre_add_sub;
24 reg [48:0]post_add_sub;

```

Flow Navigator Design

Schematic 1

Lint Checks

Filter: Type here


Waived Fixed Pending Uninspected Bug Verified Total : 17 Selected : 1

Severity	Status	Check	Alias	Message	Module	Category	State	Owner	STARC Reference
Warning	Pending	multi_ports_in_single_line		Multiple ports are declared in one line. Module Mux_R...	Mux_Reg	Rtl Design Style	open	unassig...	3.5.6.3
Warning	Pending	multi_ports_in_single_line		Multiple ports are declared in one line. Module mux2, ...	mux2	Rtl Design Style	open	unassig...	3.5.6.3
Warning	Pending	multi_ports_in_single_line		Multiple ports are declared in one line. Module mux_ci...	mux_cin	Rtl Design Style	open	unassig...	3.5.6.3
Warning	Pending	multi_ports_in_single_line		Multiple ports are declared in one line. Module mux4, ...	mux4	Rtl Design Style	open	unassig...	3.5.6.3
Warning	Pending	multi_ports_in_single_line		Multiple ports are declared in one line. Module mux4_...	mux4_x	Rtl Design Style	open	unassig...	3.5.6.3


Transcript Message Viewer Lint Checks Design Metrics Design Information Status History Lint Dashboard


6-Synthesize

Elaborated Design:

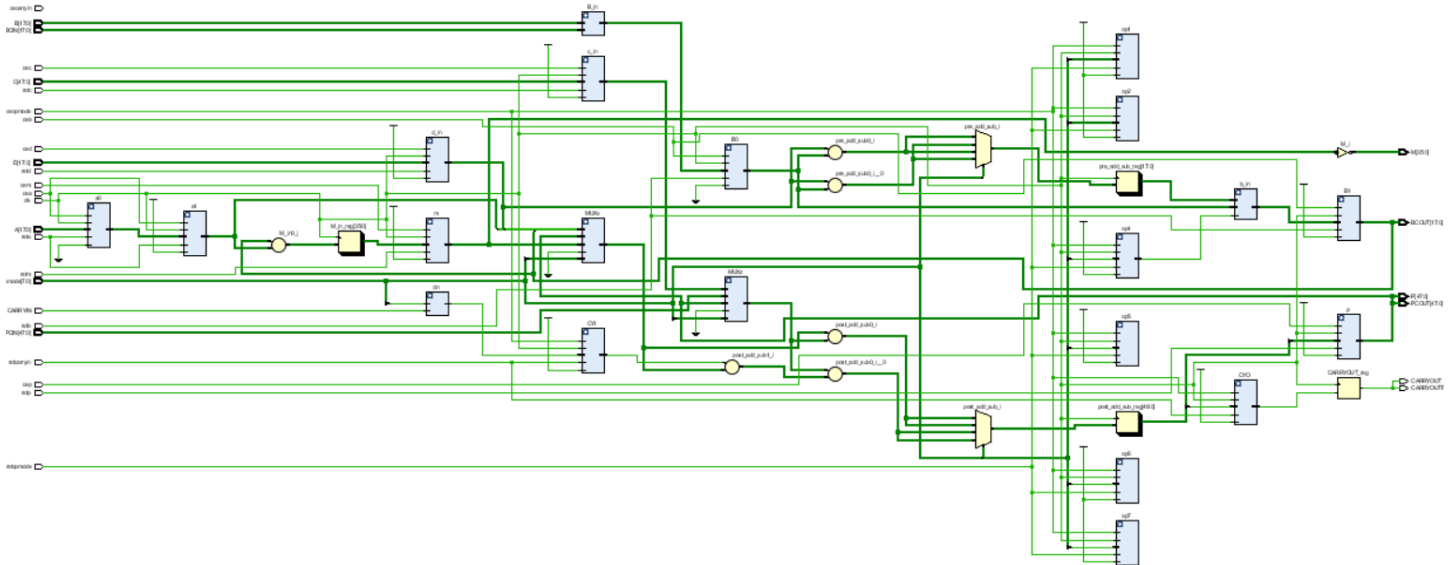

Synthesized design:

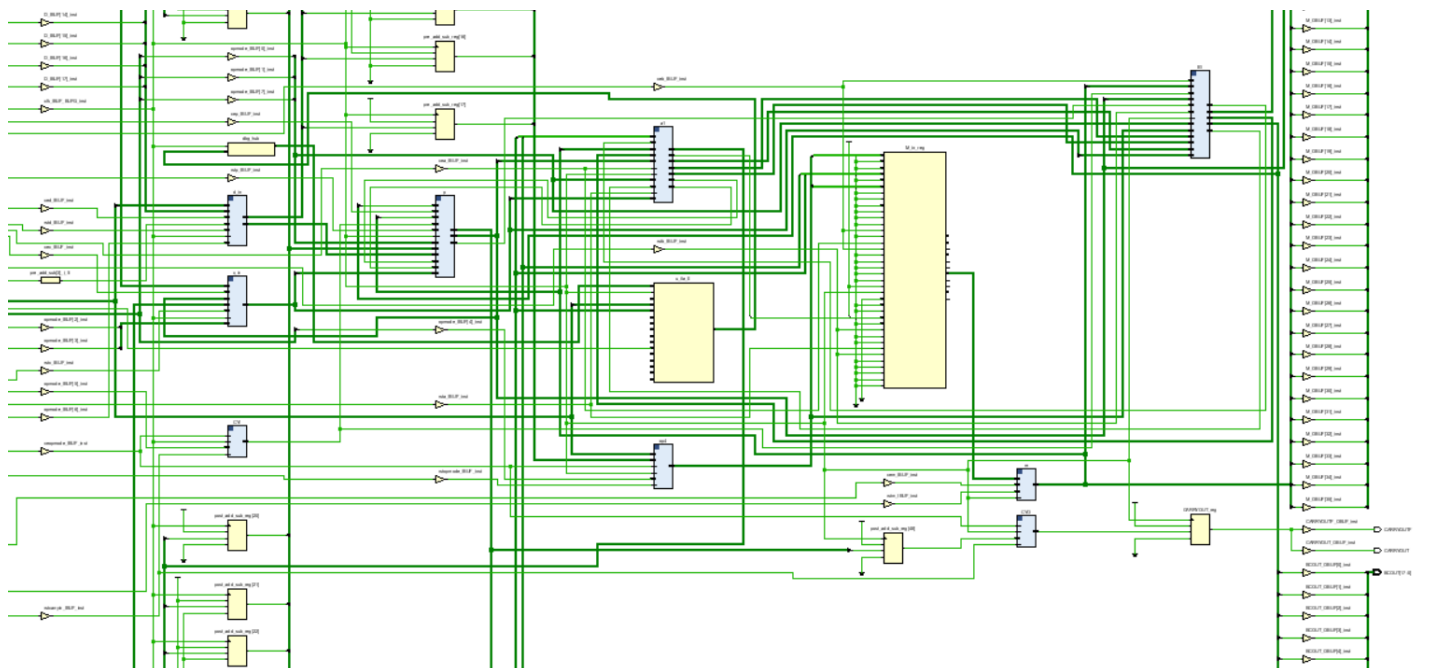

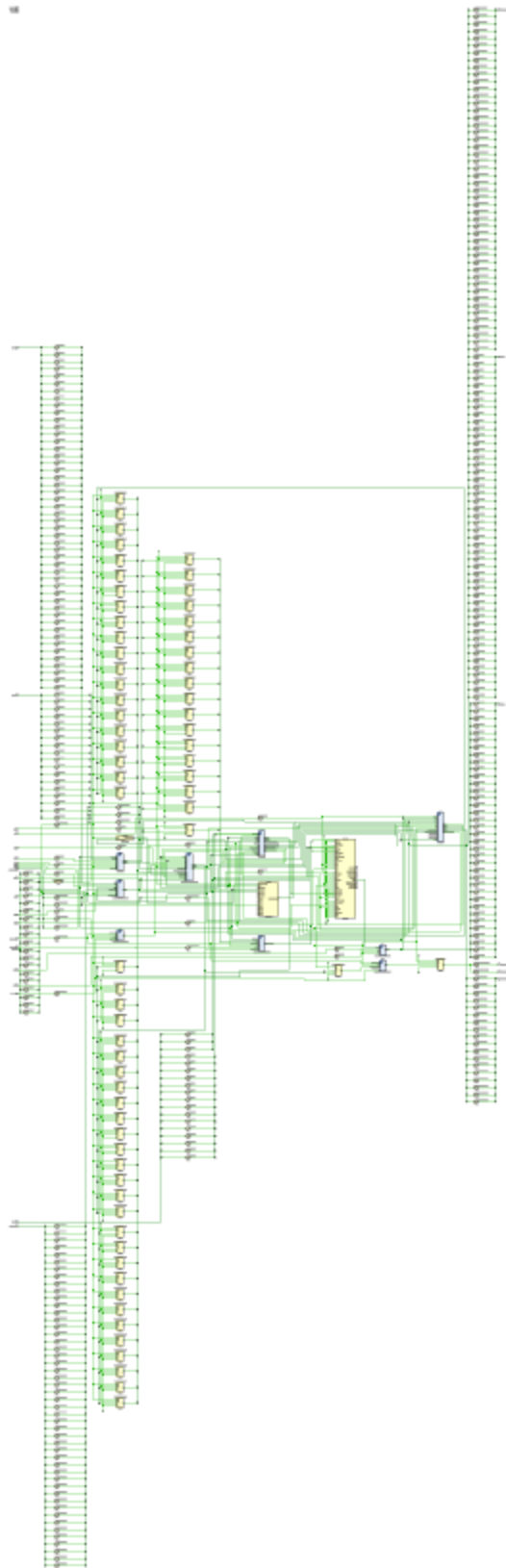

Report timing summary:

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 5.609 ns	Worst Hold Slack (WHS): 0.140 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 209	Total Number of Endpoints: 209	Total Number of Endpoints: 259


All user specified timing constraints are met.

Utilization summary:

Name	Slice LUTs (134600)	Slice Registers (269200)	DSP s (740)	Bonded IOB (500)	BUFGCTRL (32)
▼ N DSP	242	257	1	326	1
a1 (Mux_Reg_1)	54	18	0	0	0
B1 (Mux_Reg)	55	18	0	0	0
c_in (Mux_Reg__para...	48	48	0	0	0
CYI (Mux_Reg__para...	0	1	0	0	0
CYO (Mux_Reg__para...	1	1	0	0	0
d_in (Mux_Reg_2)	17	18	0	0	0
dbg_hub (dbg_hub_CV)	0	0	0	0	0
m (Mux_Reg__parame...	0	36	0	0	0
op4 (Mux_Reg__para...	18	1	0	0	0
p (Mux_Reg__paramet...	50	48	0	0	0
u_ila_0 (u_ila_0_CV)	0	0	0	0	0

Summary

Resource	Utilization	Available	Utilization %
LUT	242	134600	0.18
FF	257	269200	0.10
DSP	1	740	0.14
IO	326	500	65.20

 

7-Implementation



Report timing summary:

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 2.920 ns	Worst Hold Slack (WHS): 0.058 ns	Worst Pulse Width Slack (WPWS): 3.950 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 8088	Total Number of Endpoints: 8072	Total Number of Endpoints: 5173

All user specified timing constraints are met.

Utilization summary:

Name	Slice LUTs (133800)	Slice Registers (267600)	F7 Muxes (66900)	F8 Muxes (33450)	Slice (33450)	LUT as Logic (133800)	LUT as Memory (46200)	LUT Flip Flop Pairs (133800)	Block RAM Tile (365)	DSP s (740)	Bonded IOB (500)	BUFGCTRL (32)	BSCANE2 (4)
✓ N DSP	2671	4272	96	11	1452	2202	469	1555	8	1	326	2	1
a1 (Mux_Reg_1)	54	18	0	0	24	54	0	0	0	0	0	0	0
B1 (Mux_Reg)	55	18	0	0	20	55	0	0	0	0	0	0	0
c_in (Mux_Reg__para...	48	48	0	0	35	48	0	0	0	0	0	0	0
CYI (Mux_Reg__para...	0	1	0	0	1	0	0	0	0	0	0	0	0
CYO (Mux_Reg__para...	1	1	0	0	1	1	0	1	0	0	0	0	0
d_in (Mux_Reg_2)	17	18	0	0	12	17	0	0	0	0	0	0	0
> 3E dbg_hub (dbg_hub)	475	727	0	0	243	451	24	298	0	0	0	1	1
m (Mux_Reg__parame...	0	36	0	0	6	0	0	0	0	0	0	0	0
op4 (Mux_Reg__para...	18	1	0	0	6	18	0	0	0	0	0	0	0
p (Mux_Reg__paramet...	50	48	0	0	26	50	0	0	0	0	0	0	0
> 3E u_lla_0 (u_lla_0)	1954	3288	96	11	1122	1509	445	1181	8	0	0	0	0

Resource	Utilization	Available	Utilization %
LUT	2671	133800	2.00
LUTRAM	469	46200	1.02
FF	4272	267600	1.60
BRAM	8	365	2.19
DSP	1	740	0.14
IO	326	500	65.20

